

# Delayed Locked Loop Design Issues

**Chulwoo Kim**

ckim@korea.ac.kr

**Advanced Integrated Systems Lab**

**Korea University**

# Outline

---

- Introduction
- DLL operation and control theory
- DLL building blocks
- DLL design issues
- Multiplying DLL

# DLL vs PLL

---

- **PLL**


- VCO
  - ✓ jitter accumulation
- higher order system
  - ✓ can be unstable
- slow locking time
- hard to integrate LF
- hard to design
- + less ref. signal dependent
- + freq. multiplication
- + no limited locking range

- **DLL**

- + VCDL
  - ✓ no jitter accumulation
- + 1st order system
  - ✓ always stable
- + fast locking time
- + easy to integrate LF
- + easier to design
- ref. signal dependent
- no freq. multiplication
- limited locking range

# Jitter Accumulation Comparison


- PLL-based clock generator

 

Closed loop

- jitter accumulation

- DLL-based clock generator

 


Open loop


- No jitter accumulation
 
# Basic DLL Architectures



- Delay-locked Loop (Delay line based first order PLL)



 
- Phase-Locked Loop (VCO based second order)



# DLL Locking Process

  

# Frequency Response

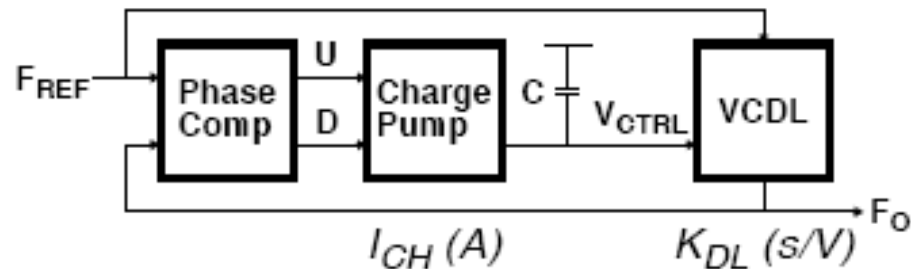

- Open loop response

$$D_O(s) = \left( \frac{D_f(s)}{T_{REF}} \cdot I_{CH} \right) \cdot \frac{1}{s \cdot C} \cdot K_{DL}$$

$$\frac{D_O(s)}{D_f(s)} = \frac{1}{s \cdot C} \cdot I_{CH} \cdot K_{DL} \cdot F_{REF} = H(s)$$

# Frequency Response(cnt'd)

---

- Closed loop response

$$D_O(s) = H(s) \cdot (D_I(s) - D_O(s))$$

$$\frac{D_O(s)}{D_I(s)} = \frac{1}{1 + \frac{1}{H(s)}}$$

$$\frac{D_O(s)}{D_I(s)} = \frac{1}{1 + \frac{s \cdot C}{I_{GH} \cdot K_{DL} \cdot F_{REF}}}$$

$$\frac{D_O(s)}{D_I(s)} = \frac{1}{1 + s/\omega_N}$$

where loop bandwidth is

$$\omega_N = I_{GH} \cdot K_{DL} \cdot F_{REF} / C$$





# Delay Cell

---

- **Single-ended delay cell**
  - Simple
  - Dynamic power only (no static current)
- **Differential delay cell**
  - Complex biasing
  - Static power consumption
  - Immune to supply noise and thus smaller jitter
- **Variables for delay control**
  - Current
  - Capacitance
  - Resistance
  - Voltage swing
- **Fine delay generation**
  - Phase interpolation
  - Vernier delay line



# Single-Ended Delay Cell

- Current-starved inverter delay line

  


# Single-Ended Delay Cell(cnt'd)

- Capacitor-loaded inverter delay line

  
 
# Single-Ended Delay Cell(cnt'd)


- Inverters with regulated supply voltage



[S. Sidiropoulos, SOVC00]
 
# Differential Delay Cell


- Differential delay element with resistive loads



- High power supply rejection ratio
- Requirements
  - ✓ Adjustable loads to control the delay and resistive loads to reject power supply noise
 
# Differential Delay Cell(cnt'd)


- Voltage-controlled two-element PFET “Resistor”



- Adjustable load :  $I_{load} = B_p (V_c - V_{tp})^2$
- Resistive load : S-shaped, nearly resistive
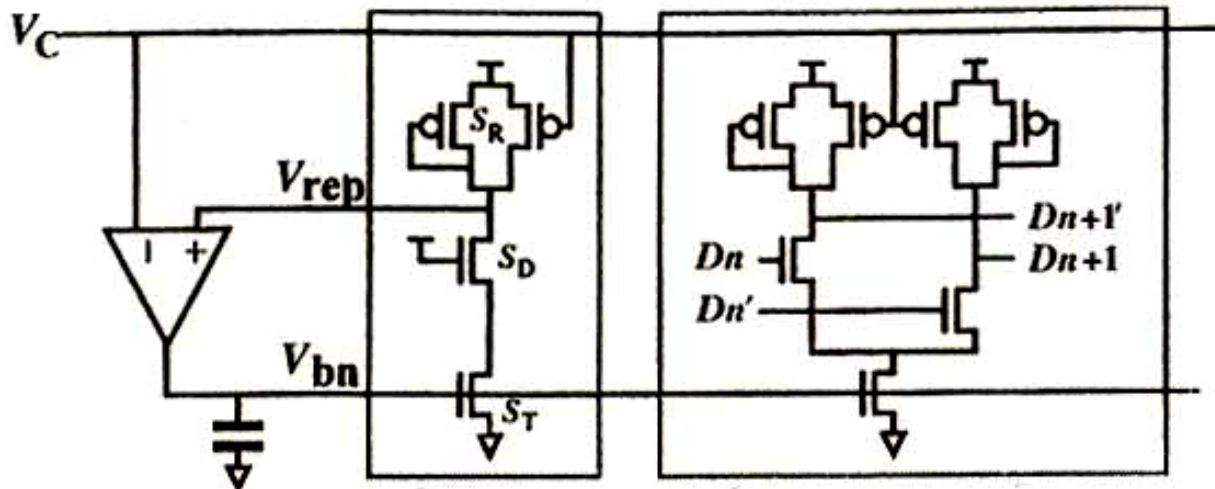
# Differential Delay Cell(cnt'd)


- Replica-biased differential delay line circuitry




- The low end of the signal swing can be set by controlling the bias current with a replica bias circuit

# Differential Delay Cell(cnt'd)

- Replica-biased delay line

 

 
(a) Delay adjustment range for replica-biased delay element



(b) Static supply sensitivity for replica-biased delay element




# Phase Interpolation

 

- Can interpolate between two edges through a weighted sum
  - Control over delay is guaranteed to be monotonic, but not necessarily linear
    - ✓ Resolution can be arbitrarily high
    - ✓ Precision is limited by linearity

# Delay Line Vernier


 


$$\text{Delay} = n \cdot t_d \cdot (1 + 1/N) + (N - n) \cdot t_d = (N + n/N) \cdot t_d$$





- Can use two delay lines with switches to use part of one and remainder of the other with fractionally larger delays  $(1 + 1/N)$ 
  - Delay resolution is a buffer delay  $/ N$
  - Relative precision is limited by control over  $t_x / t_y$
  
# Phase Detector

- **Output describes phase difference between two inputs**
  - may be analog or digital
  - may linearly cover a wide range, or just a narrow phase difference
  - “Dead zone” may occur




# Phase-Frequency Detector

  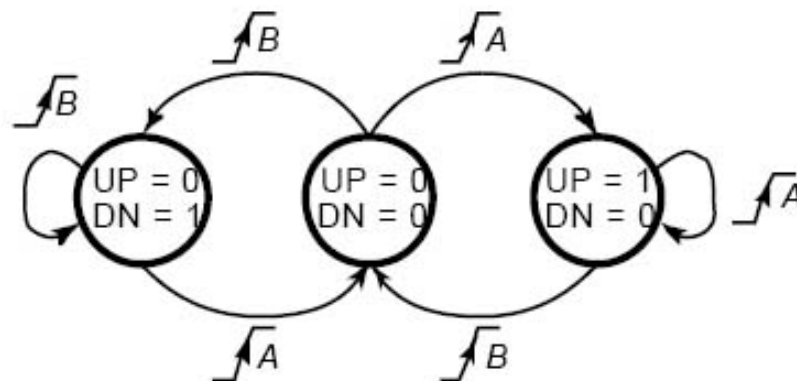 

 
# Dead-Zone in PFD

- “Dead-zone” occurs when the loop doesn’t respond to small phase errors - e.g. 10 ps phase error at PFD inputs:
  - Solution: delay reset to guarantee min. pulse width (typically > 100 ps)


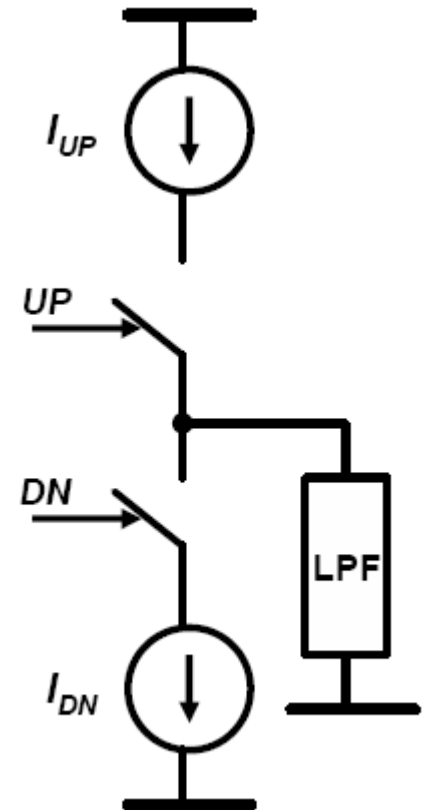
# Charge Pump


- Converts PFD digital *UP/DN* signals into charge
- Charge is proportional to duration of *UP/DN* signals
- $Q_{cp} = I_{UP} * t_{UP} - I_{DN} * t_{DN}$
- The LPF converts integrates currents
- Charge pump requirements:
  - Match currents *IUP* and *IDN*
  - Reduce control voltage coupling
  - Supply noise rejection, PVT insensitivity  
(Simple or bandgap biased)




# Charge Pump: Better Switches

- Unity-gain buffer controls the voltage over switches
- Current mirrored into  $I_{up}/I_{dn}$

Young, JSSC 12/92

 


# Charge Pump: Zero-Offset

 

- Up and down nodes track with each other thanks to the self-bias scheme.




# Charge Pump : Reversed Switches

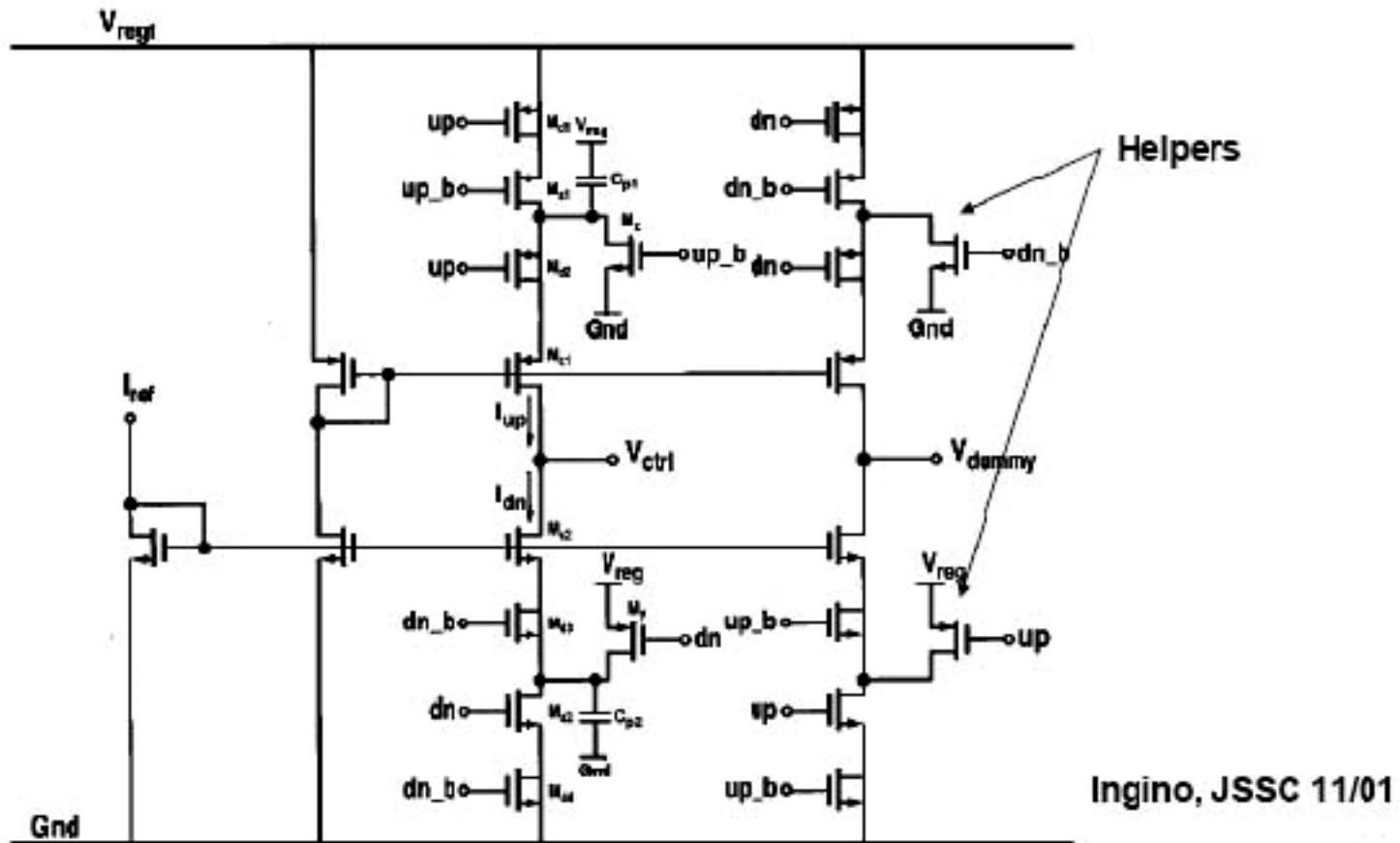



# 2<sup>nd</sup> Order Charge-Pump Scheme : Mismatch Cancellation

2nd order charge pump block


 


[K. Kim, ISSCC 04]



1st order (Conventional)

  

2nd order (Original)

  

2nd order (Hybrid)

  

# Design Issues

---

- **Bandwidth**
- **Limited lock range**
- **Lock in time**
- **Static phase offset**
- **Power dissipation limits**
- **Area limits**
- **Peak output jitter**

# Bandwidth

---

- **Bandwidth**

- A wider loop bandwidth

- ✓ Fast acquisition time but degraded jitter performance

- $$\frac{\omega_N}{F_{REF}} = \frac{I_{CH} \cdot K_{DL}}{C} \leq \frac{\pi}{5} \quad [A. Chandrakasan, IEEE Press, 2001]$$


- $I_{CH}$ ,  $K_{DL}$ , and  $C$  are process technology dependent.

- According to the design target, the loop bandwidth varies.

# Adaptive Bandwidth

- Self-biased DLL

[J. Maneatis, JSSC 96]

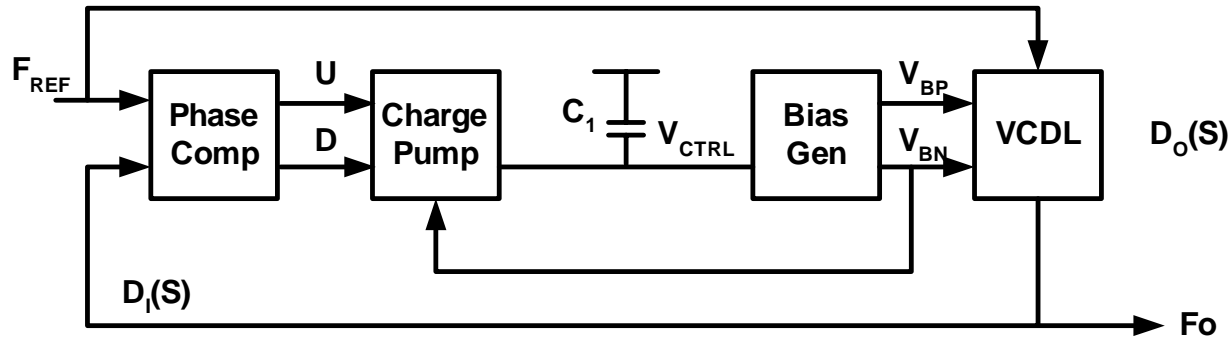

## Current and gain of VCDL

$$I_D = \frac{k}{2} \cdot (V_{CTRL} - V_T)^2 \quad K_{DL} = \frac{C_B}{4 \cdot I_D}$$


## Current of Charge pump

$$I_{CH} = x \cdot (2 \cdot I_D)$$

$$\begin{aligned} \frac{\omega_N}{\omega_{REF}} &= \frac{1}{\omega_{REF}} \cdot I_{CH} \cdot K_{DL} \cdot F_{REF} \cdot \frac{1}{C_1} \\ &= \frac{1}{2\pi} \cdot I_{CH} \cdot K_{DL} \cdot F_{REF} \cdot \frac{1}{C_1} \\ &= \frac{1}{2\pi} \cdot x \cdot (2 \cdot I_D) \cdot \frac{C_B}{4 \cdot I_D} \cdot \frac{1}{C_1} \\ &= \frac{1}{4\pi} \cdot \frac{C_B}{C_1} \end{aligned}$$

# Locking Range

- Locking range

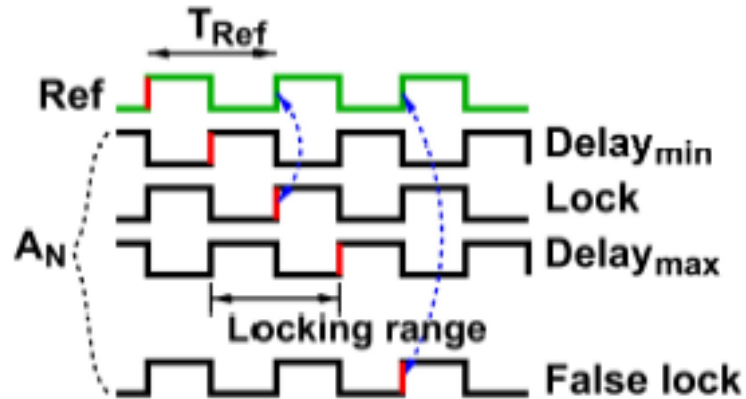



$$0.5 \times T_{CLK} < T_{VCDL_{\min}} < T_{CLK}$$

$$T_{CLK} < T_{VCDL_{\max}} < 1.5 \times T_{CLK}$$


$$\text{Max}(T_{VCDL_{\min}}, 2/3 \times T_{VCDL_{\max}}) < T_{CLK} < \text{Min}(2 \times T_{VCDL_{\min}}, T_{VCDL_{\max}})$$

# Harmonic Lock Problem

- Correct and false locking

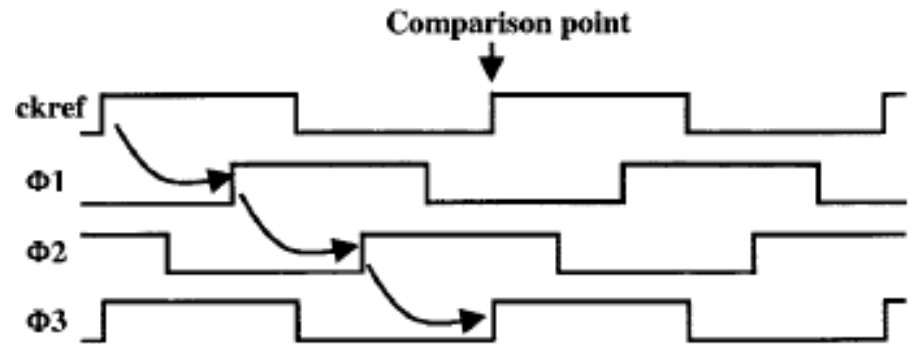 


Correct locking

 

False locking

# DLL Locking Using Inversion

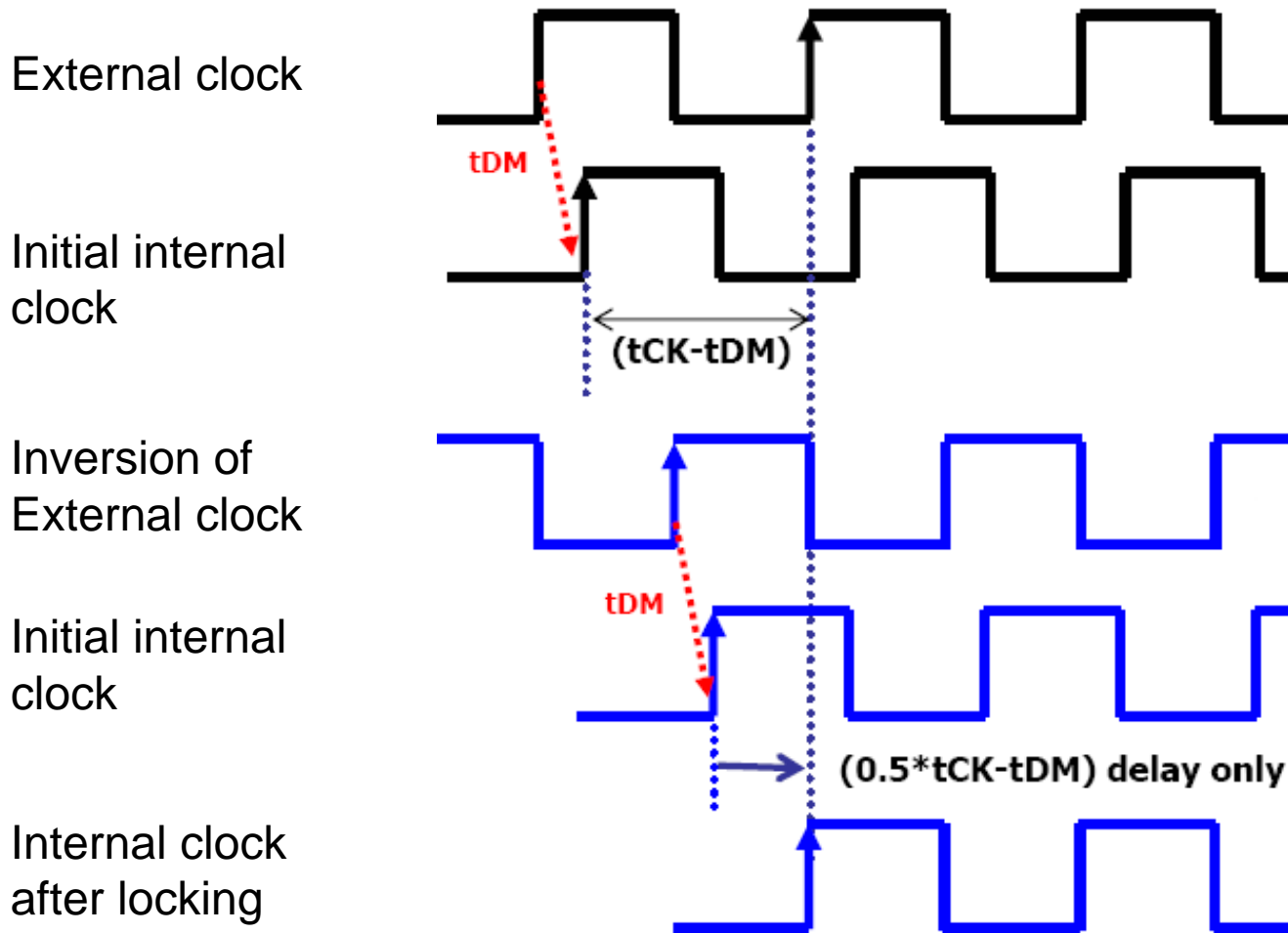




# Wide Range DLL

---

- **Overcome the false locking problem**
  - Rotating phase DLL
  - Phase detector which can detect harmonic locking
  - Initial locking starts within delay range
- **Widen operating frequency**
  - Using multiple phases

# Rotating Phase DLL


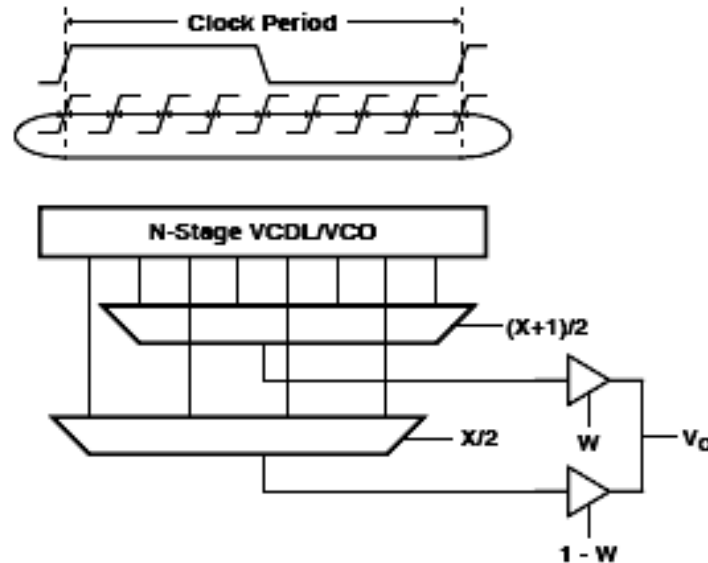


- Uses N-stage VCDL or VCO phase-locked to clock period as timing reference to supply output phases that are uniformly distributed over clock period
- Selects or interpolates output phases from delay reference
- Unlimited output phase range (modulo clock period)

# Rotating Phase DLL (cnt'd)



## Semi-digital DLL

[S. Sidiropoulos, JSSC97]

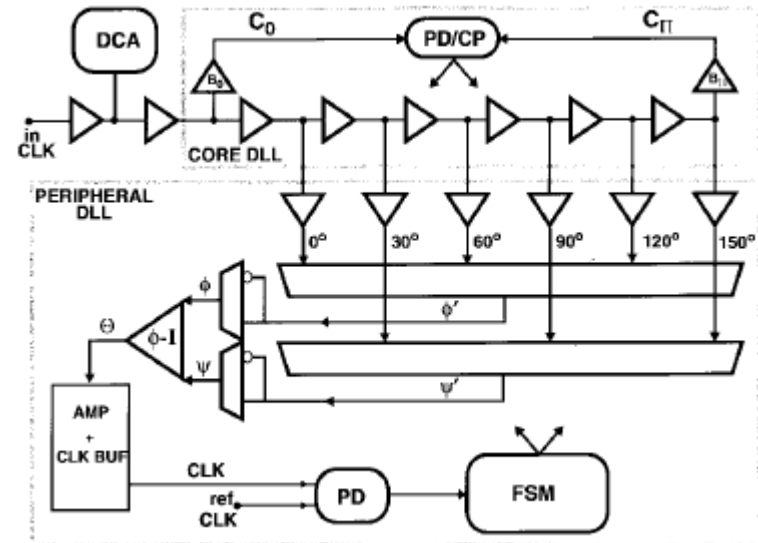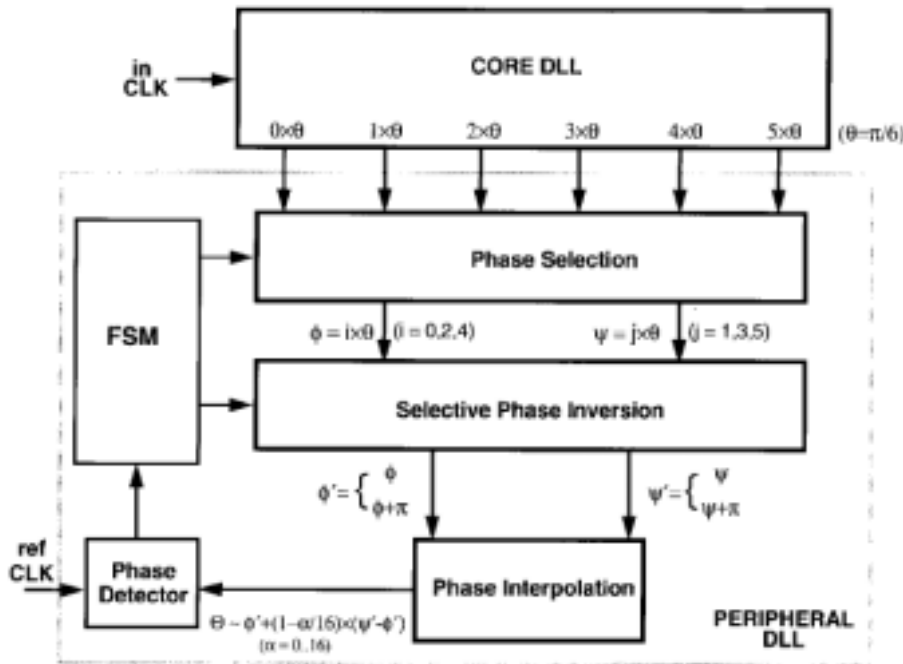


# Self-Correction DLL

[D.J.Foley, JSSC01]

 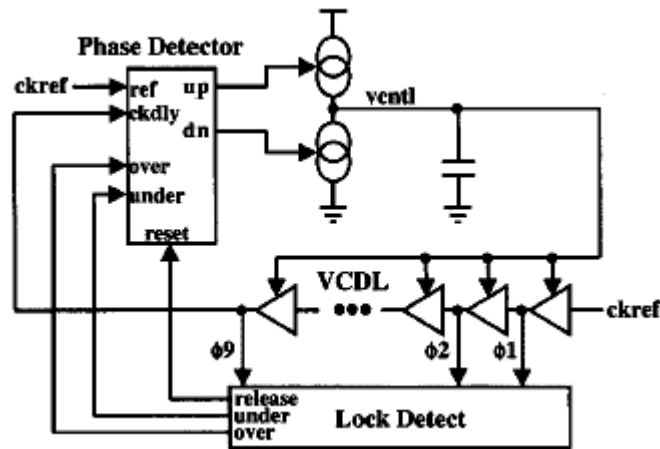

Correct locking


 


False locking

- Phase detector gains the control of loop according to release, under and over


# DLL Using A Replica Delay Line

[Y.Moon, JSSC00]

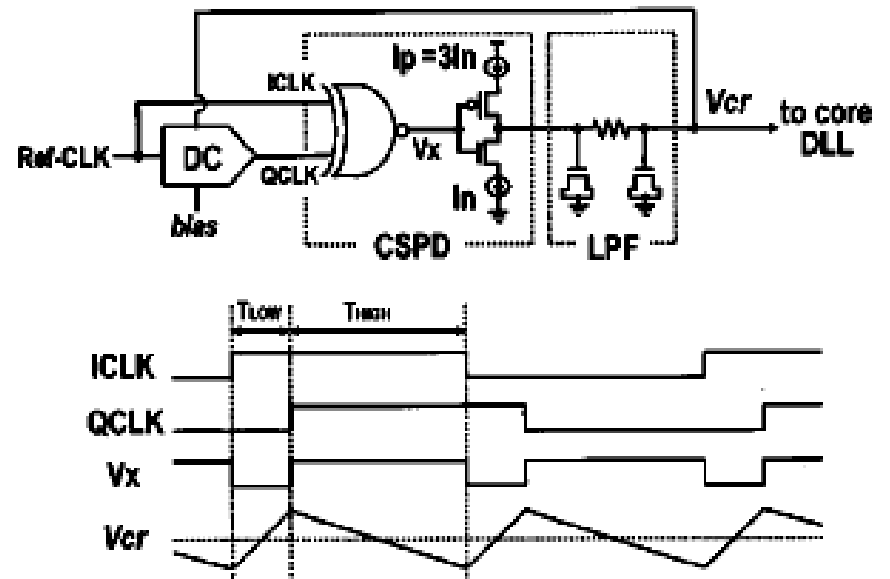
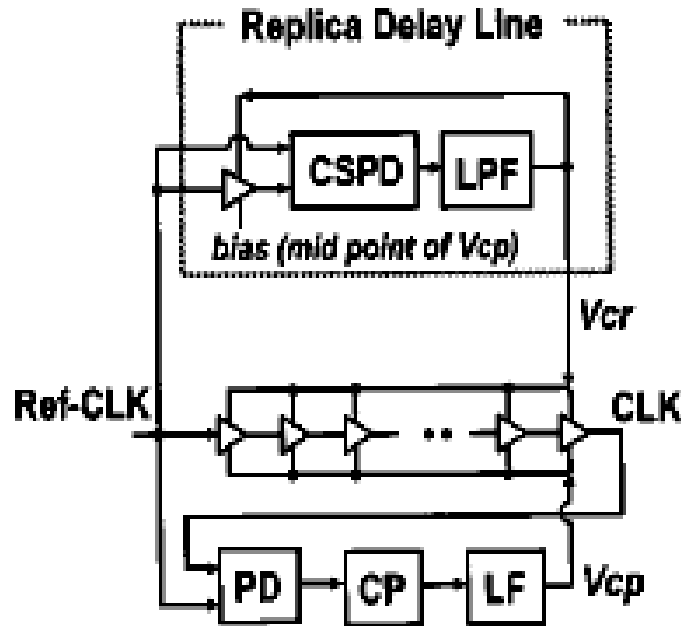


- The control voltage of RDL protect false locking

# DLL Using Multiple Phases

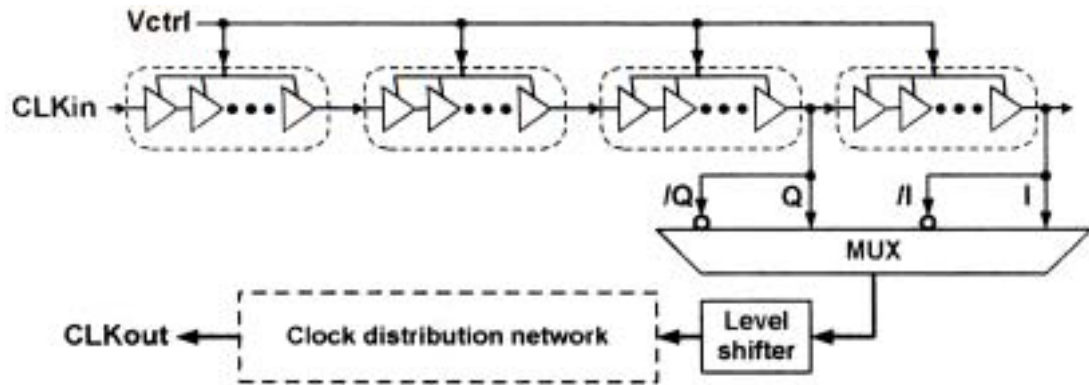

[B.Kim, CICC04]

  


# Lock Time

---

- **Lock time limits (< 100 cycles for DDR)**
  - Need high tracking bandwidth ( self-biased DLLs)
  - Digital DLLs can use “non-linear” techniques
  - Open loop

# Digital Delay Line DLL

 


- Uses digital delay line with fixed delay as timing reference
- Selects output phases from delay reference (digital control)
- Correction step size is typically fixed
  - Large locking time (clock cycle · number of steps)
  - Can use exponentially decreasing steps (SADLL)
- Digital delay control provides more flexibility



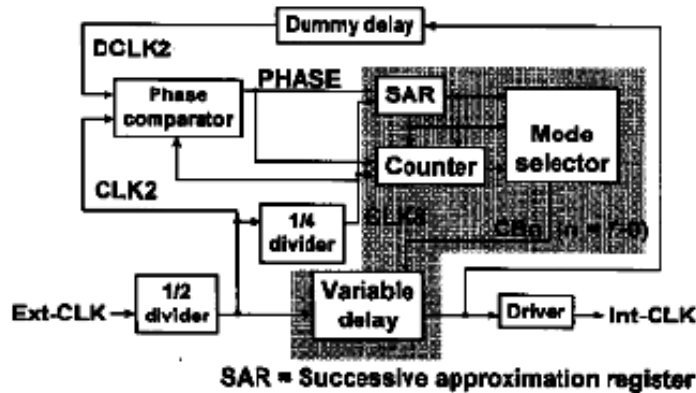
# Digital Delay Line DLL with SAR

- Successive Approximation Register DLL [M.Hasegawa, ISSCC98]




- Fast-lock by successive approximation < 64 cycles
- Counter-mode operation during normal cycle


During lock-in

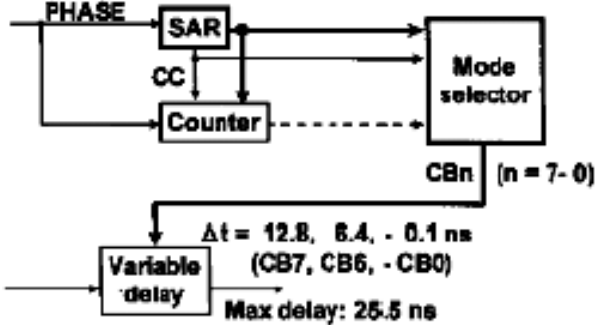

After lock-in

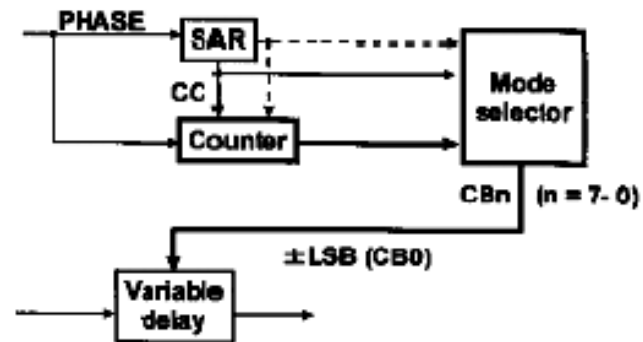


# Digital Delay Line DLL with SAR(cnt'd)

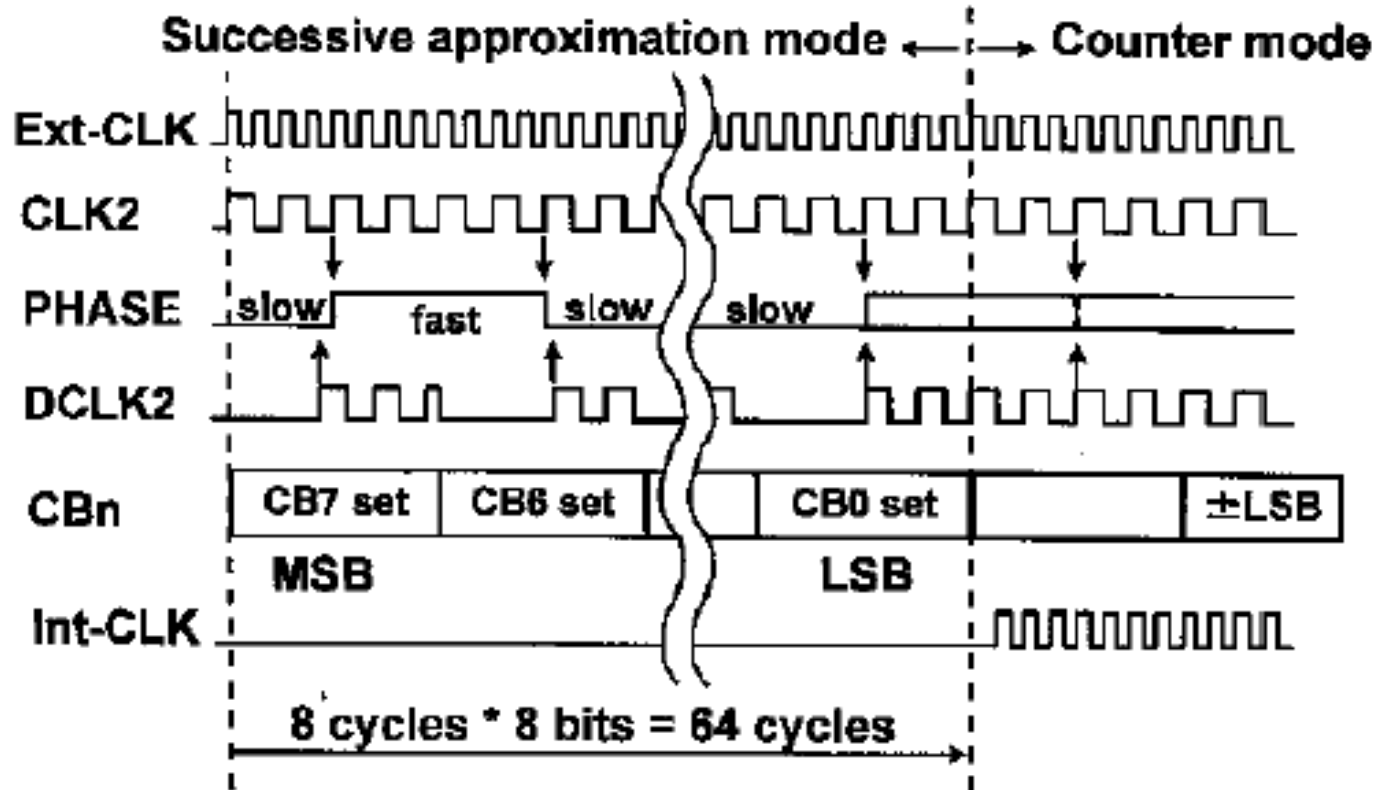


# All-Digital DLL Using a TDC

[C.Chung, JSSC04]

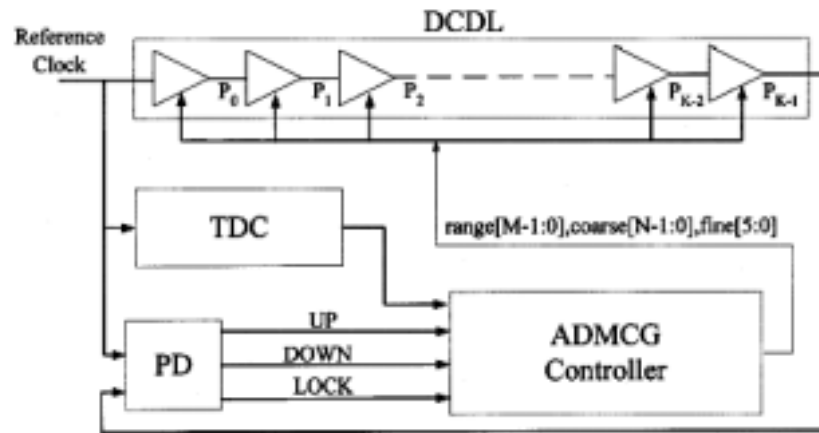


Overall architecture

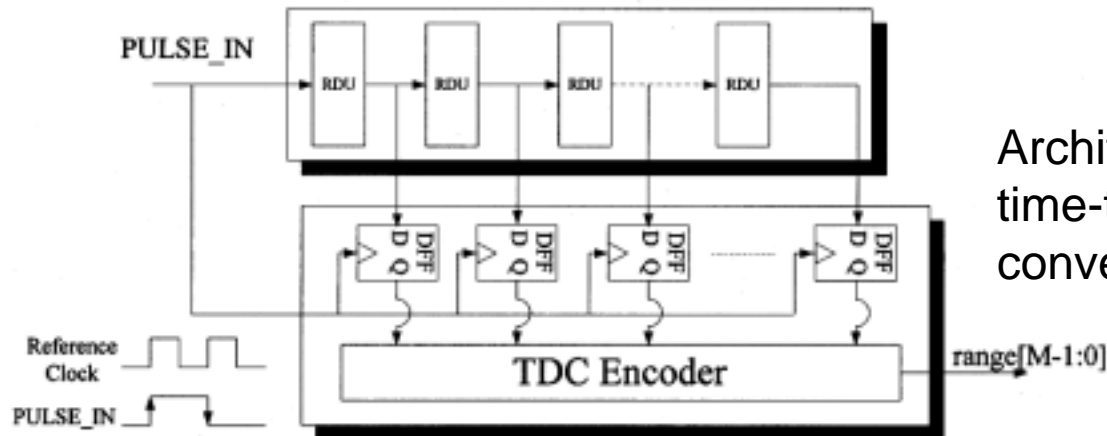

Architecture of the time-to-digital converter (TDC)


# Schematic of Dual Coarse Delay Line

[J. Kwak, SOVC03]

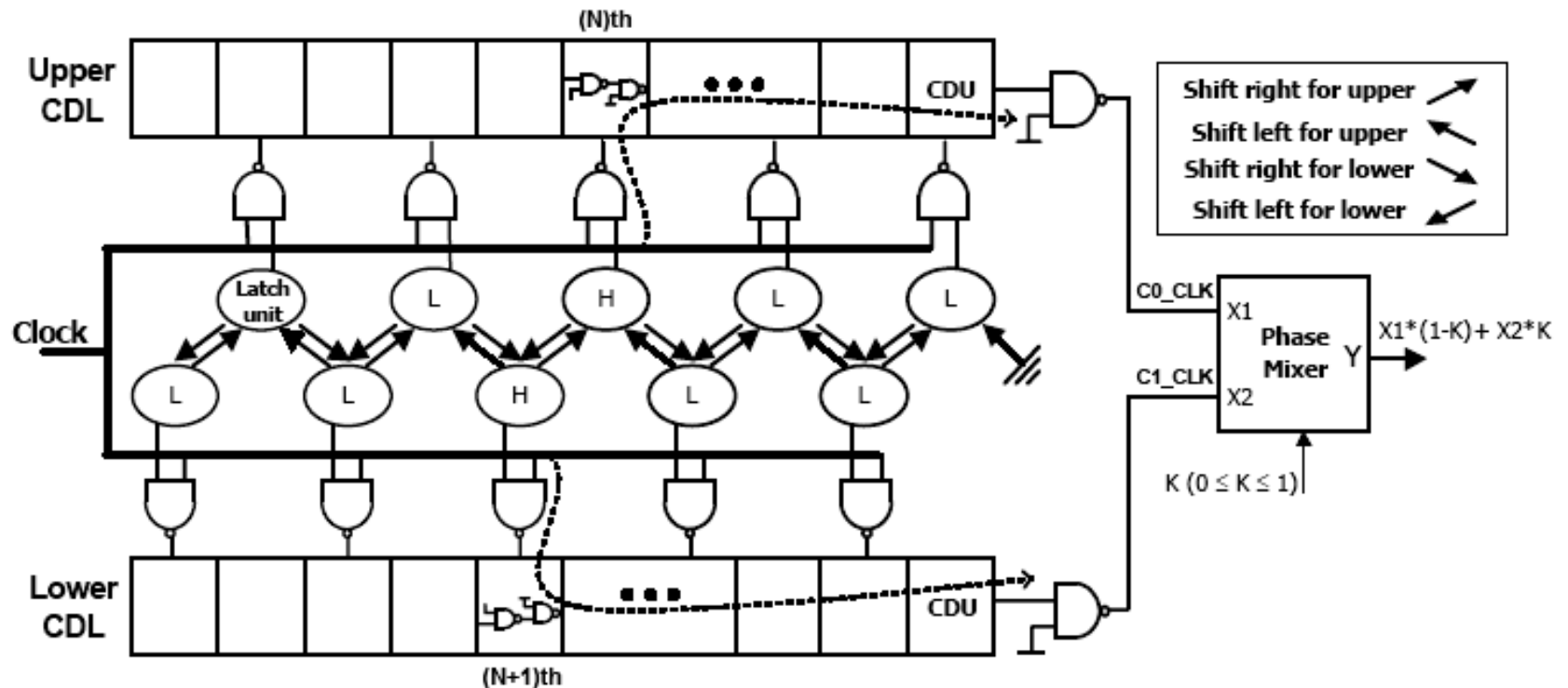

# Compensation of Static Phase Offset

[B.Kim, CICC04]

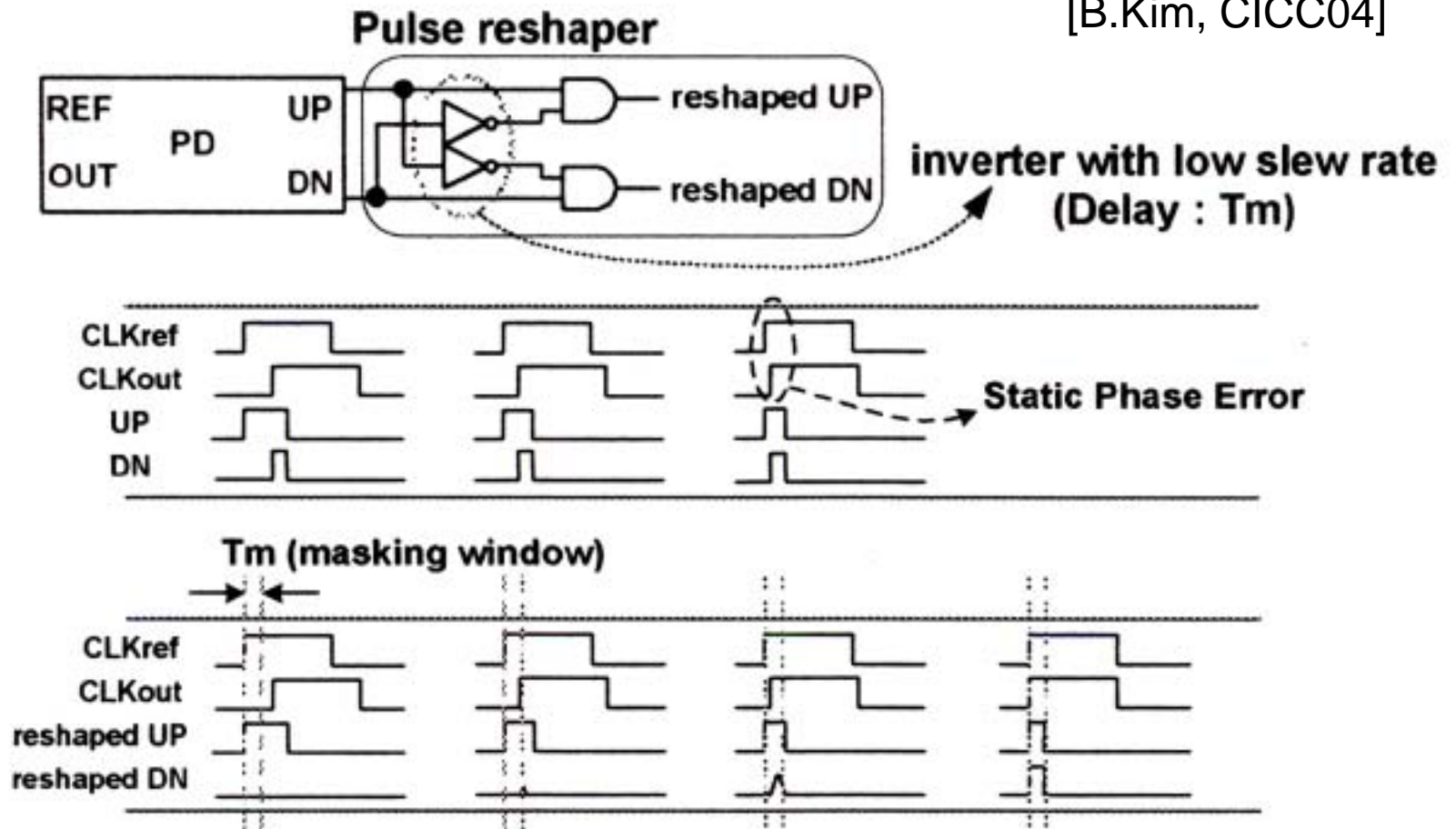


# Power Dissipation and Area

---

- **Power dissipation limits**
  - **Operating power**
    - ✓ **Analog DLLs can use less power than digital DLLs**
  - **Stand-by power**
    - ✓ **Analog DLLS cannot be turned off for long without relocking (charge in loop filter cap. Will leak away)**
    - ✓ **Digital DLLs store locked state in registers**
- **Area limits**
  - **Analog DLLs can have smaller area than digital DLLs**
    - ✓ **Digital delay line DLLs that support low operating frequencies can be very large**

# Register Controlled DLL


[A.Hatakeyama, ISSCC97]

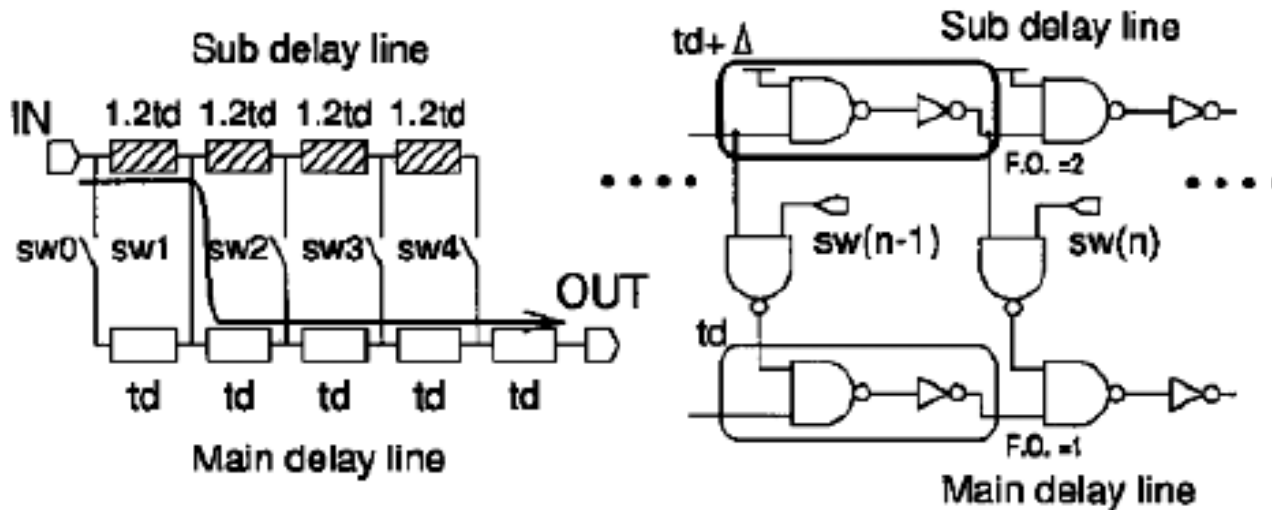

- Locking information is stored as a digital code.
- High resolution because of vernier type delay line.

# Portable DLL

[B.W.Garlepp, JSSC99]

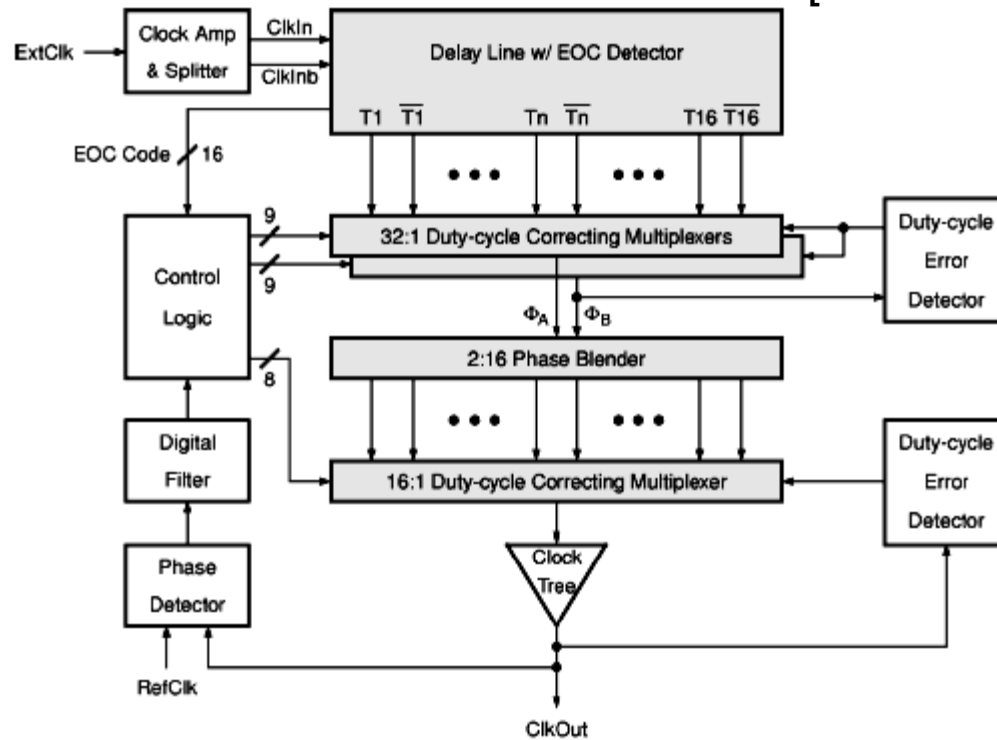


- Phase information is stored in control logic.




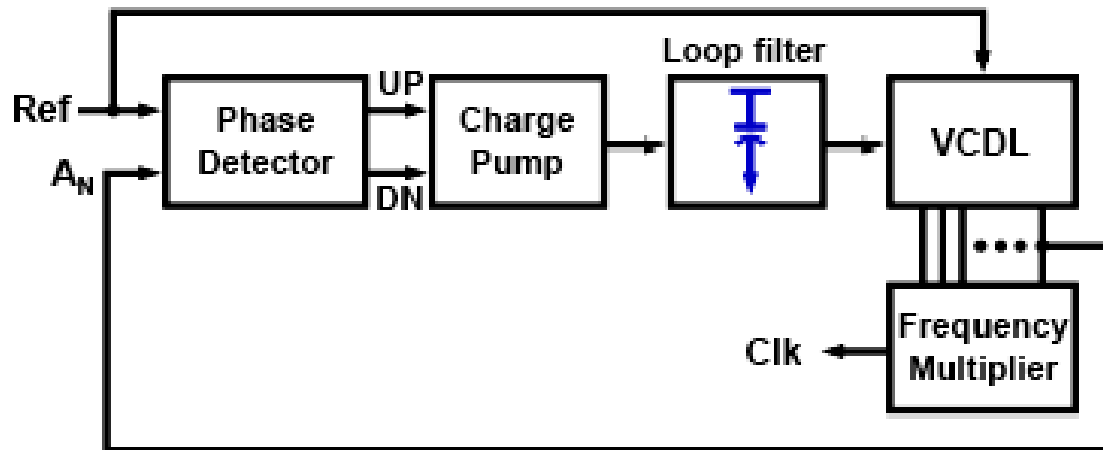
# Multiplying DLL

- Avoid jitter accumulation problem of PLL without VCO
- 1<sup>st</sup>-order system
  - Stable and easier to design
- Block diagram




# Multiplying DLL With LC tank

 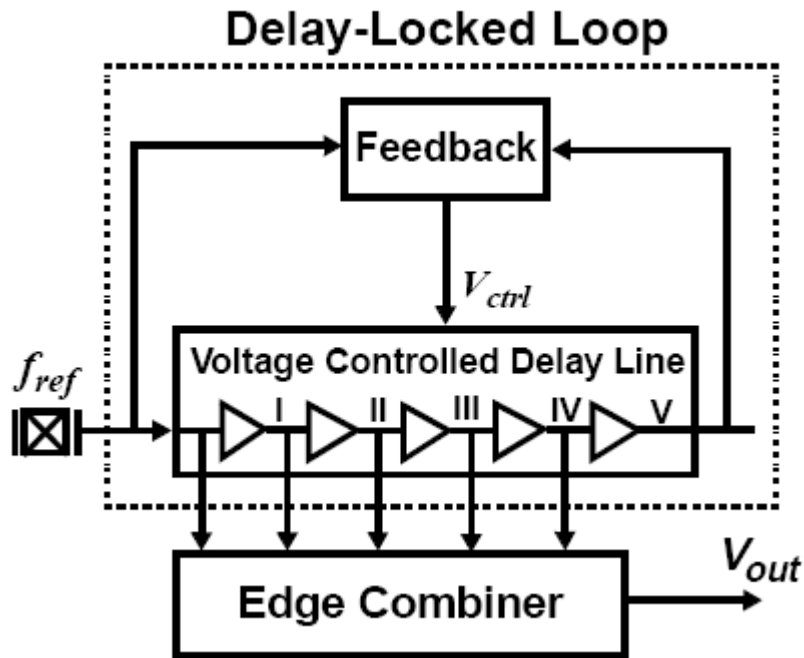

[G. Chien, JSSC 2000]


# Multiplying DLL With LC tank (cnt'd)

 

- Diff. pair modulates tail currents into LC-tank circuit
- LC-Tank enhances load impedance : large area & fixed multiplication ratio
- Large current necessary for large voltage swing


# Multiplying DLL With AND/OR Gate

[D.J.Foley, JSSC 2001]

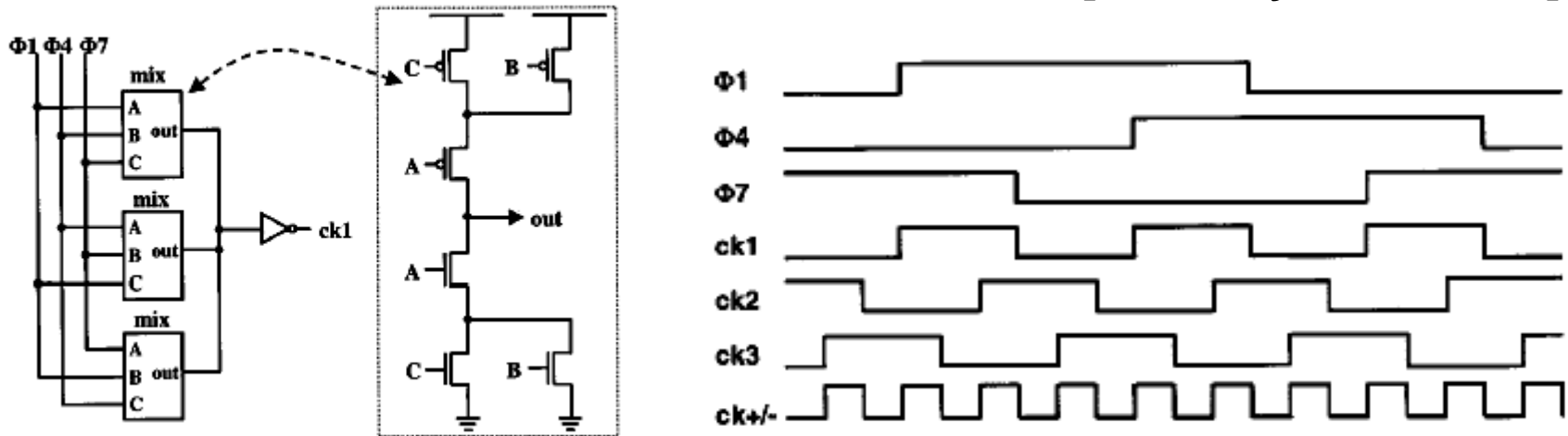


- AND/OR gate: 9 times freq. multiplication
- Need analog OR I/O buffer & 50 pull-up resistor: off-chip clock signal

# Multiplying DLL With Digital Controls

 



[C.Kim, JSSC 2002]

 

- Low power and small area
- Easier to integrate
- Multiplication factor can be easily programmable

# Multiplying DLL for Low-jitter Clock Generation

[R. Farjad-Rad, JSSC 2002]

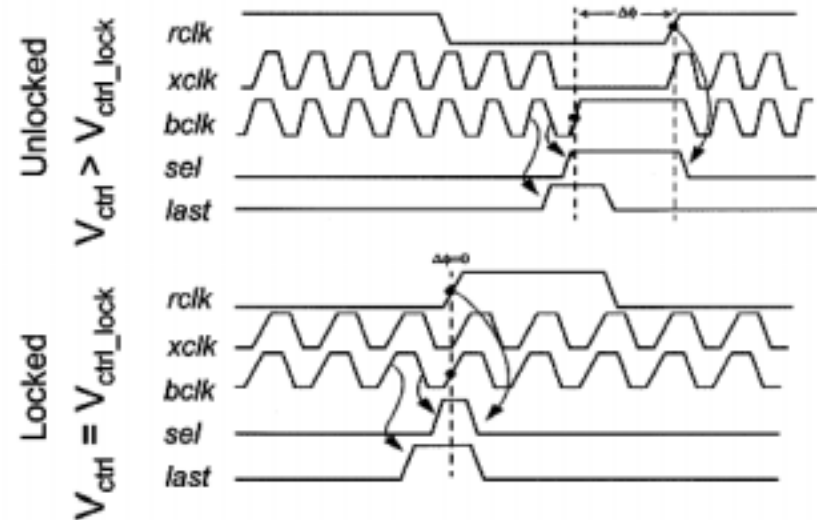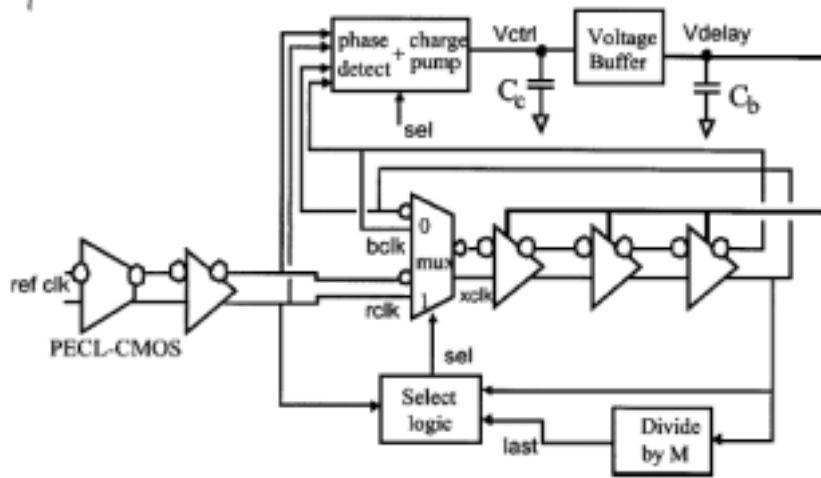

# Conclusions

---

- **As data rates increase, DLLs will become essential to relax system timing constraints in each direction of data transfer.**
- **DLL consists of phase detector, voltage controlled delay cell, loop filter and charge pump.**
- **DLL should be designed as considering below issues.**
  - **Bandwidth**
  - **Limited lock range**
  - **Lock in time**
  - **Power dissipation limits**
  - **Area limits**
  - **Peak output jitter**

# References

- [S.Sidiropoulos SOVC 2000] S. Sidiropoulos, D. Liu, J. Kim, G. Wei, and M. Horowitz, "Adaptivebandwidth DLL's and PLL's using regulated supply CMOS buffers," in *VLSI Symp. Dig. Tech. Papers*, June 2000, pp. 124–127.
- [Young JSSC 1992] I.A. Young; J.K Greason; K.L Wong, "A PLL clock generator with 5 to 10MHz of lock range for microprocessors," *IEEE J. Solid-state Circuits*, vol. 27, no. 11, pp1599-1607
- [Ingino JSSC 2001] J.M. Ingino, V.R von Kaenel, "A 4-GHz clock system for a high-performance system-on-a-chip design" *IEEE J. Solid-state Circuits*, vol. 36, no. 11, pp1693-1698
- [K. Kim ISSCC 04] K. Kim *et al* , "1.4Gb/s DLL using 2<sup>nd</sup> order charge-pump scheme with low phase/duty error for high-speed DRAM application" *ISSCC 2004 Dig. Tech. Papers*, pp 212-213, Feb 2004
- [A. Chandrakasan, IEEE Press, 2001] A. Chandrakasan, W. J. Bowhill, and F. Fox, *Design of High-Performance Microprocessor Circuit*. New York: IEEE Press, 2001, p. 240.
- [J. Maneatis, JSSC Nov 96] J. Maneatis, "Low-Jitter Process-Independent DLL and PLL Based on Self-Biased Techniques," *IEEE J. Solid-State Circuits*, vol. 31, no. 11, pp. 1723-1732, Nov. 1996.
- [S. Sidiropoulos, JSSC Nov 97] S. Sidiropoulos, and M. Horowitz, "A semidigital dual delay-locked loop," *IEEE J. Solid-State Circuits*, vol. 32, no. 11, pp. 1683-1692, Nov. 1997.
- [D.J. Foley JSSC] D.J.Foley and M.P.Flynn, "CMOS DLL-based 2-V 3.2-ps jitter 1-GHz clock synthesizer and temperature-compensated tunable oscillator," *IEEE J. Solid-State* , vol. 36, pp.417-423, Mar. 2001
- [Y.Moon JSSC 2000] Y. Moon, J. Choi, K. Lee, D. K. Jeong, and M. K. Kim, "An all-analog multiphase delay-locked loop using a replica delay line for wide-range operation and low-jitter performance," *IEEE J. Solid-State Circuits*, vol.35, pp. 377–384, Mar. 2000.
- [B.Kim, CICC04] B.Kim and L. Kim, "A 250MHz-2GHz wide range delay-locked loop," In *Proc.IEEE CICC 2003*, pp.139-142, Oct 2004.
- [M. Hasegawa, ISSCC98] M. Hasegawa, et al., "A 256Mb SDRAM with subthreshold leakage current suppression," *ISSCC 1998 Dig. Tech. Papers*, pp. 80-81, Feb. 1998.
- [C.Chung, JSSC04] C. Chung and C. Lee "A New DLL-Based Approach for All-Digital Multiphase Clock Generation" *IEEE J. Solid-State Circuits*,vol. 39, pp 469-475, MAR. 2004
- [J. Kwak, SOVC03] J.Kwak *et al.*"A low cost high performance register-controlled digital DLL for 1 Gbps\_spl times\_32 DDR SDRAM" *Symp. VLSI Circuits Dig. Tech. Papers*, pp283-284, 2003
- [A. Hatakeyama ISSCC 1997] A. Hatakeyama, H. Mochizuki, T. Aikawa, M. Takita, Y. Ishii, H. Tsuboi, S. Fujioka, S. Yamaguchi, M. Koga, Y. Serizawa, K. Nishimura, K. Kawabata, Y. Okajima, M. Kawano, H. Kojima, K. Mizutani, T. Anezaki, M. Hasegawa, and M. Taguchi, "A 256 Mb SDRAM using register-controlled digital DLL," in *ISSCC 1997 Dig. Tech. Papers*, Feb.1997, pp. 72–73.
- [B.W Garlepp JSSC 99] B.W. Garlepp, K. S. Donnelly, J. Kim, P. S. Chau, J. L. Zerbe, C. Haung, C. V. Tran, C. L. Pourtman, D. Stark, Y. Chan, T. H. Lee, and M. A. Horowitz, "A portable digital DLL for high-Speed CMOS interface circuits,"*IEEE J. Solid-State Circuits*, vol. 34, pp. 632–644, May 1999.
- [V. von Kaenel, ISSCC98] V. von Kaenel, et al., "A 600MHz CMOS PLL microprocessor clock generator with a 1.2GHz VCO," *ISSCC 1998 Dig. Tech. Papers*, pp. 396-397, Feb. 1998.
- [G. Chien , JSSC 2000] G. Chien and P. R. Gray, "A900-MHz local oscillator using a DLL-based frequency multiplier technique for PCS applications," *IEEE J. Solid- State Circuits*, vol. 35, pp. 1996–1999, Dec. 2000.
- [C. Kim, JSSC 2002] C. Kim, I.-C. Hwang, and S.-M. Kang, "A low-power small-area  $\pm 7.28$ -ps-jitter 1-GHz DLL-based clock generator," *IEEE J. Solid-State Circuits*, vol. 37, no. 11, pp. 1414-1420, Nov. 2002.
- [R. Farjad-Rad, JSSC 2002] R. Farjad-Rad *et al.*, "A low-power multiplying DLL for low-jitter multigigahertz clock generation in highly integrated digital chips," *IEEE J.Solid-State Circuits*, vol. 37, pp. 1804–1812, Dec. 2002.[J. Kwak, SOVC03] J.Kwak *et al.*"A low cost high performance register-controlled digital DLL for 1 Gbps\_spl times\_32 DDR SDRAM" *Symp. VLSI Circuits Dig. Tech. Papers*, pp283-284, 2003